

①

# Digital Logic Design

bse  
133

## Assignment # 02

Name: AOUN-HAIDER

ID: FA21-BSE-133

∴ |—————| ∴

(2.2)

Minimize literals:

$$a) xy + xy'$$

$$= x(y + y')$$

$$= x(1)$$

$$\Rightarrow x$$

$$b) (x+y)(x+y')$$

$$= x + xy' + xy + yy'$$

$$= x + xy' + xy + 0$$

$$= x + x(y+y')$$

$$= x + x(1)$$

$$= x$$

$$c) xyz + x'y + xyz'$$

$$= xy(z + z') + x'y$$

$$= xy + x'y$$

$$= y(x + x')$$

$$= y$$

$$d) (x+y)'(x'+y)'$$

Apply De-morgan's law

$$= (x'y')(xy)$$

$$= 0$$

②  
BS E-13

$$e) (a+b+c')(a'b'+c)$$

$$= aa'b' + ac + a'bb' + cc'$$

$$= (0)b' + ac + a'(0) + 0$$

$$\Rightarrow ac$$

$$f) a'bc + abc' + abc + a'bc'$$

$$= a'bc + ab(c'+c) + a'bc'$$

$$= ab + a'bc + a'bc'$$

~~$$ab + bc + a$$~~

$$= ab + a'b(c+c')$$

$$= ab + a'b$$

$$= (a+a')b$$

$$\Rightarrow b$$

2.4

$$a) x'y'z' + y + xy'z'$$

$$= (x' + x) y'z' + y$$

$$\Rightarrow y'z + y$$

Reduce to minimum number of literals

~~$$x'y'z + x'z$$~~

$$b) x'y(x' + z') + x'y + xyz$$

$$= xy + x'y'z' + x'y + xyz$$

$$= (x + x')y + x'y'z' + xyz$$

$$= y + y(x'z' + xz)$$

$$\Rightarrow y$$

BSE-133

Verification by K-maps

x \ yz	00		01		11		10	
	0	1	2	3	4	5	6	7
0	0	0	1	1	0	0	0	0
1	0	0	1	1	0	0	0	0

= y

x	y	z	F	
0	0	0	0	
0	0	1	0	2
0	1	0	1	3
0	1	1	1	
1	0	0	0	
1	0	1	0	6
1	1	0	1	7

$$\begin{aligned}
 c) & (x+yz)' + (x+y'z')' \\
 &= (x')(y'+z') + (x')(y+z) \\
 &= x'y' + x'z' + x'y + x'z \\
 &= x'(y'+y) + x'z' + x'z \\
 &= x' + x'z' + x'z \\
 &= x'(1+z'+z) \\
 &= x'
 \end{aligned}$$

BSE-133

$$\begin{aligned}
 d) & (w'+x)(w+y)(x'+y)(w+xyz) \\
 &= (w'w + w'y + xw + xy)(x'+y)(w+xyz) \\
 &= (x'w'y + w'y + x\cancel{w}w + xwy + x\cancel{x'y} + xy)(w+xyz) \\
 &= (x'w'y + w'y + xwy + xy)(w+xyz) \\
 &= x'w'y + x\cancel{x'}w'y + w\cancel{w}'y + w'y^2 + xwy + xwy^2 + xwy + xy^2
 \end{aligned}$$

$$= w'y^2 + x\cancel{w}y + xwy^2 + xy^2$$

$$\begin{aligned}
 e) & wx'y'z' + wy' + w\cancel{x}'y'z' \\
 &= wy'z'(x+x') + wy' \\
 &= wy'z' + wy'
 \end{aligned}$$

(2.6)


Draw circuit of simplified equations in 2.3.

a)  $xy^2 + x'y + xy^2' \rightarrow \text{simplified: } y$


c)  $x'y' \leftarrow (x+y)'(x'+y')$

f)  $(x'+z')(x+y'+z')$

a)

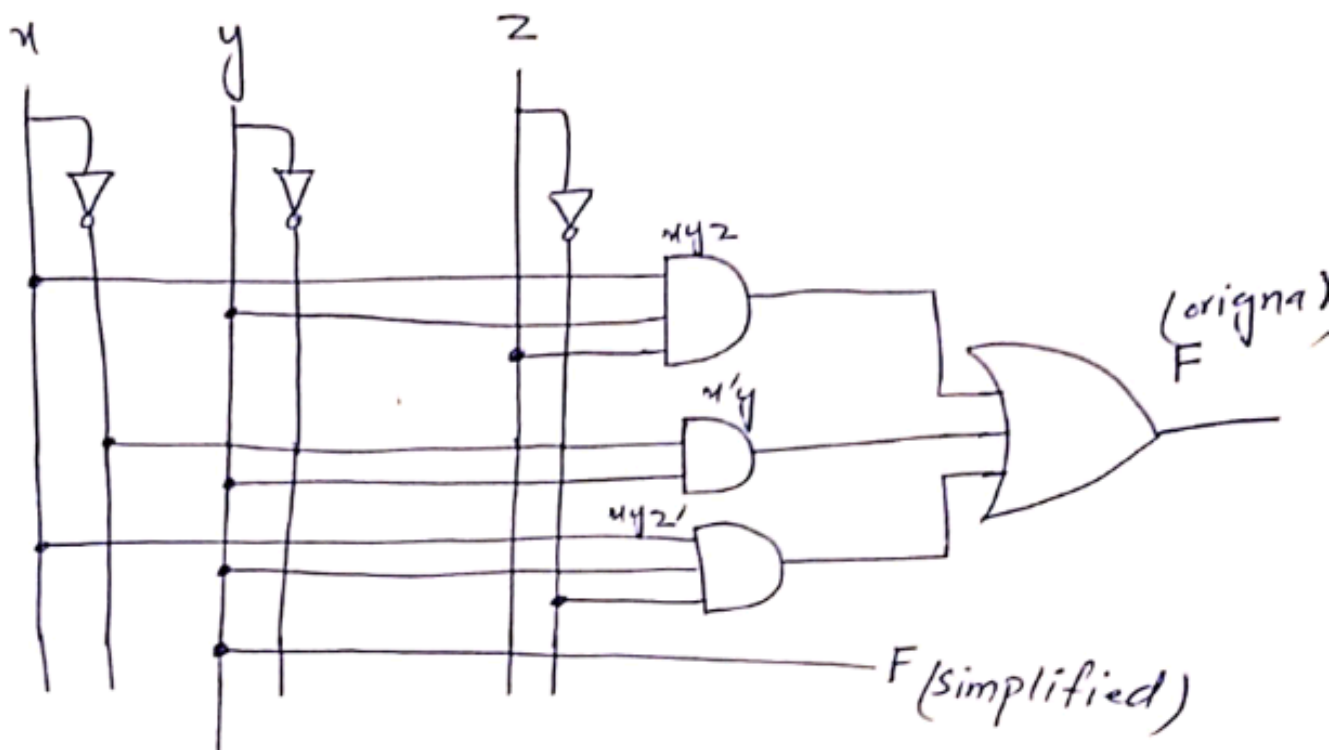


b)

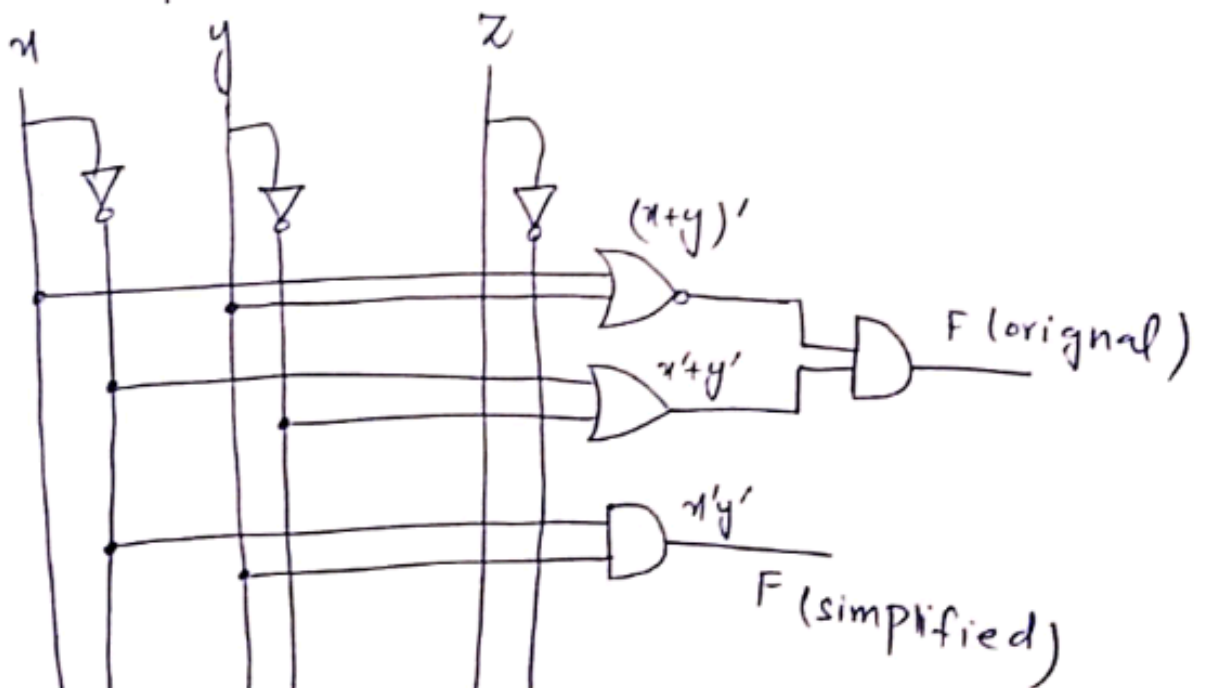



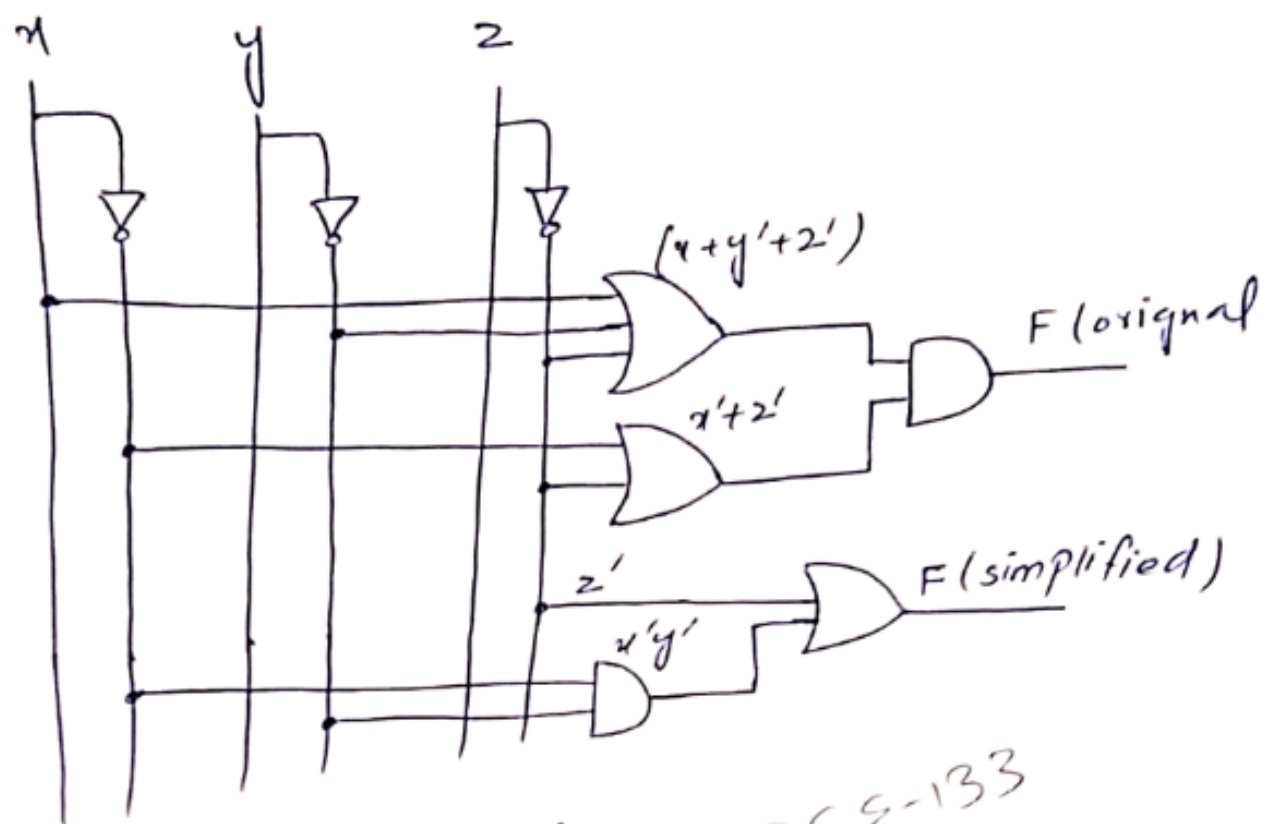7)  $(x + y' + z')(x' + z') = \text{original}$   
 $z' + x'y' = \text{simplified}$



(2.8)

BSE-133

Find Complement

$$F = x'y + yz'$$

Show that  $FF' = 0$  &  $F + F' = 1$

$$F' = (x'y + yz')'$$

$$= (x'y)'(yz')' \Rightarrow (x + y')(y' + z)$$

$$\begin{aligned} \textcircled{1} FF' &= (x'y + yz')(x + y')(y' + z) \\ &= x'xy + x'y/y' + xy2' + yxy'z' \\ &= xy2'(y' + z) \\ &= xy y'z' + xy2z' \Rightarrow 0 + 0 = 0 \end{aligned}$$

$$(2) F + F' = 1$$

$$\begin{aligned} F + F' &= x'y + yz' + (x+y')(y'+z) \\ &= x'y + yz' + xy' + xz + \bar{y} + y'z \\ &= y(1+z') + z(x+y') + x'y + xy' \\ &= y + x'y + xy' + xz + xy' \\ &= y + x'y + xy' + xz \\ &\quad \text{OR} \\ &= x'y + yz' + (x'y + yz')' \\ &= 1 + 0 \\ &\quad \text{OR} \\ &= 0 + 1 \\ \boxed{F + F' = 1} \end{aligned}$$

(2.10)

Show that

$$E = F_1 + F_2$$

$$G = F_1 F_2$$

$$a) \text{ Let } F_1 = \overset{4}{0} \overset{2}{x'} \overset{1}{y} \overset{0}{z'} + \overset{1}{x'} \overset{1}{y} \overset{1}{z} + \overset{0}{x'} \overset{2}{y} \overset{1}{z} = \Sigma(2, 3, 7)$$

$$F_2 = \overset{1}{x} \overset{1}{y} \overset{0}{z'} + \overset{0}{x} \overset{1}{y} \overset{1}{z} + \overset{0}{x} \overset{0}{y} \overset{0}{z} = \Sigma(0, 3, 6)$$

$$E = F_1 + F_2 = \overset{4}{0} \overset{2}{x'} \overset{1}{y} \overset{0}{z'} + \overset{1}{x} \overset{1}{y} \overset{0}{z'} + \overset{0}{x} \overset{1}{y} \overset{1}{z} + \overset{4}{x} \overset{2}{y} \overset{0}{z'} + \overset{4}{x} \overset{2}{y} \overset{1}{z}$$

$$= \overset{4}{0} \overset{2}{x'} \overset{1}{y} \overset{0}{z'} + \overset{1}{x} \overset{1}{y} \overset{0}{z'} + \overset{0}{x} \overset{1}{y} \overset{1}{z} + \overset{4}{x} \overset{2}{y} \overset{0}{z'} + \overset{4}{x} \overset{2}{y} \overset{1}{z}$$

$$= \Sigma(0, 2, 3, 6, 7) \rightarrow \text{contains min terms of } F_1 \& F_2$$

b)

$$G = F_1 F_2 = (x'yz' + xy2 + x'y2)$$

$$(xy2' + x'y2 + x'y'2')$$

$$= x'x'yz' + x'y22' + x'y y'2' + xy22' + x'x'y2 + x'y y'22' + xx'y22' + x'y2 + x'y y'22'$$

$$= x'y2$$

=  $\Sigma(3) \rightarrow$  the common term in both min terms.

(2.12)

Apply logical operators:

A = 11001010 , B = 10010011

a) AND    b) OR    c) XOR    d) NOT A

A	B	AND	OR	XOR	NOT A
1	1	1	1	0	0
1	0	0	1	1	0
0	0	0	0	0	1
0	1	0	1	1	0
1	0	0	1	1	0
0	1	0	1	1	1
1	1	1	1	0	0
0	1	0	1	1	1

AND  $\Rightarrow$  10000010

OR  $\Rightarrow$  10011011

XOR  $\Rightarrow$  01011001

NOT A  $\Rightarrow$  00110101




(2.14)

Implement boolean function

$$F = x'y + xy' + xz$$


a) with AND, OR & inverter gate

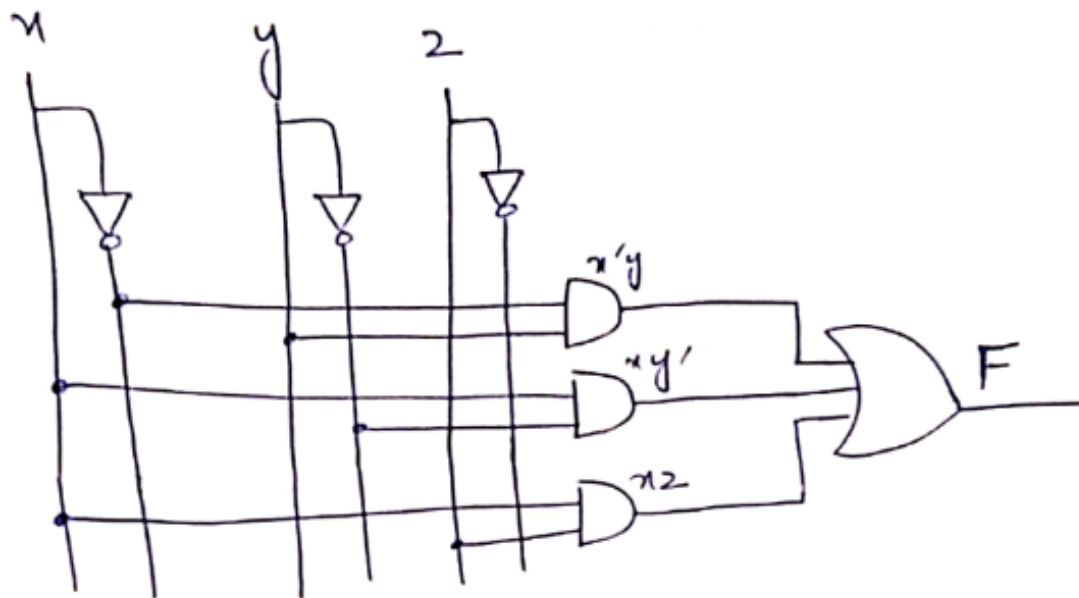

b) With OR & inverter only

Apply De-morgan's law

$$= (x + y')' + (x' + y)' + (x' + z')'$$

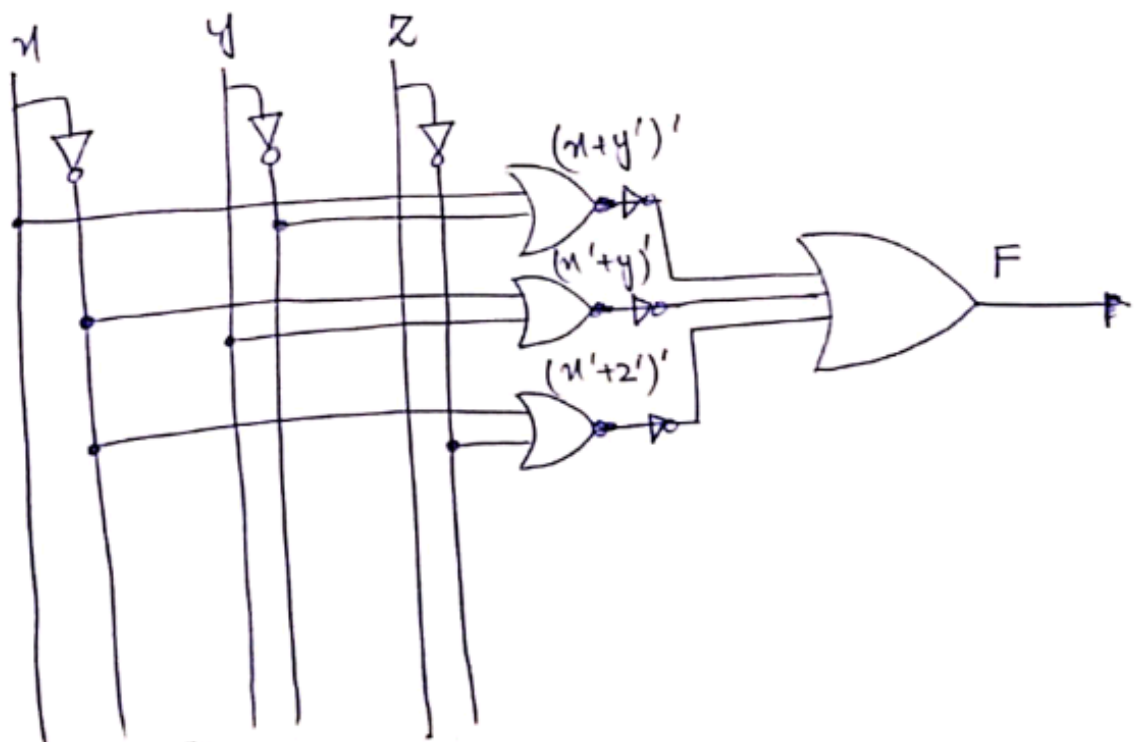


c) With AND and inverter

(10)

$$F = x'y + xy' + xz$$


$$F = [(x'y)'(xy')'(xz)']'$$

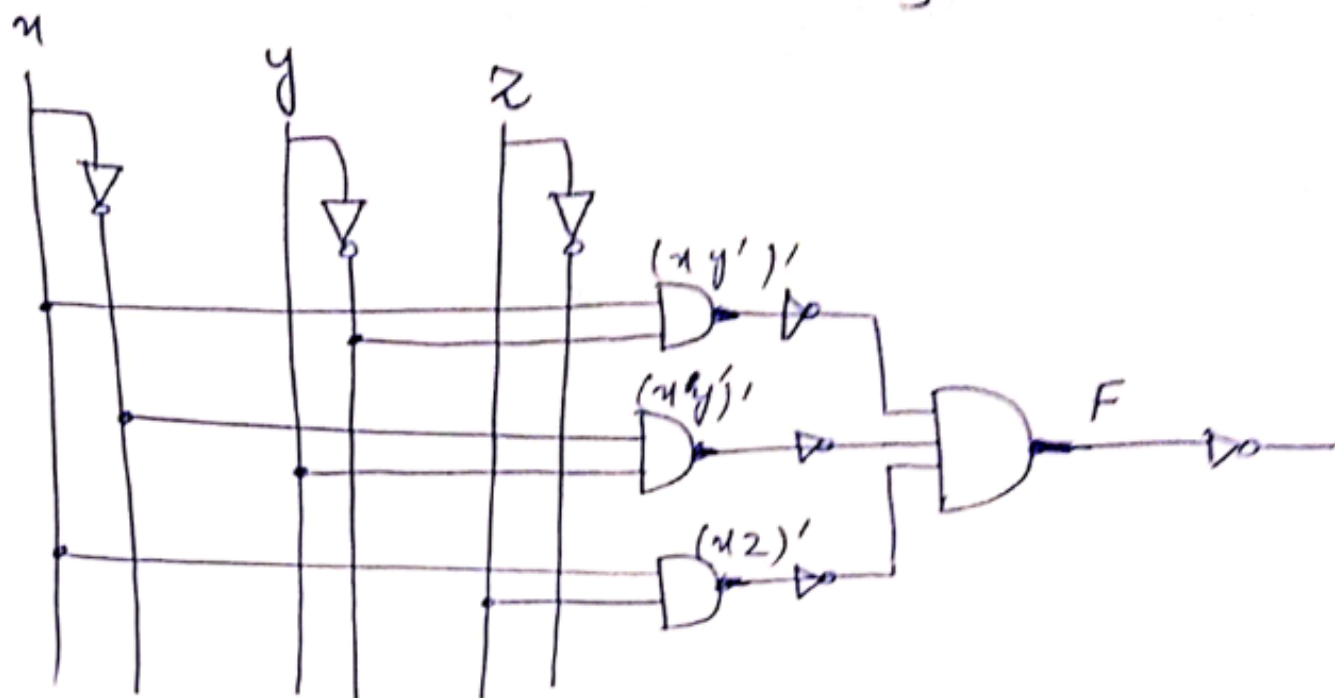

d) With NAND and inverter


$$F = x'y + xy' + xz$$

$$F = [(x'y)'(xy')'(xz)']'$$

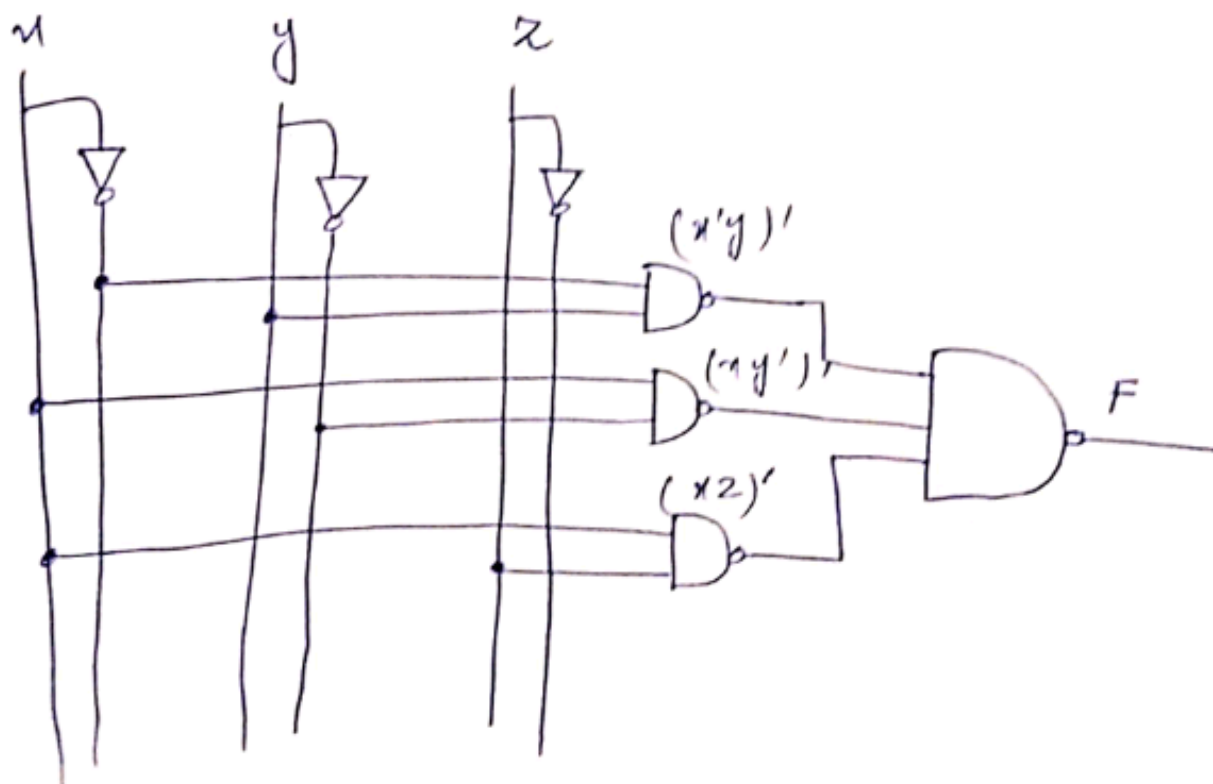

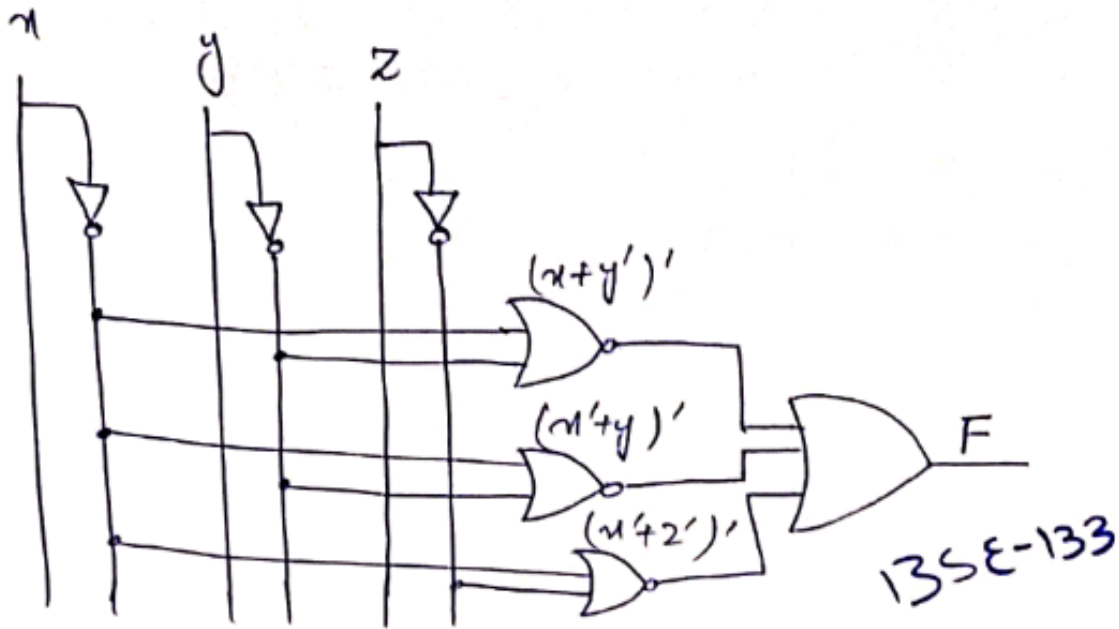e) NOR & inverter  

$$F = x'y + xy' + xz = (x+y')' + (x'+y)' + (x+z)'$$



(2.16)

Logical sum of all minterms = 1

a) prove when  $n=3$

$$\sum m_i = 1 \text{ where } i=3$$

Let input variables are  $x, y$  &  $z$

$$F(x, y, z) = x'y'z' + x'y'z + x'yz' + x'yz + xy'z' + xy'z + xyz' + xyz$$

$$= x'(y'z' + y'z + yz' + yz) + x(y'z' + y'z + yz' + yz)$$

$$= (x' + x)(y'z' + y'z + yz' + yz)$$

$$= y'z' + y'z + yz' + yz$$

$$= y'(z' + z) + y(z' + z)$$

$$= (y' + y)(z' + z)$$

$$= 1$$

$$F(x_1, x_2, x_3, \dots, x_n) = \sum m_i$$

$\sum m_i$  has  $2^n$  no. of terms

①  $\sum m_i$  has  $(\frac{2^n}{2})$  minterms with  $x_1$  &  $\frac{2^n}{2}$  will have  $x_1'$  which can be factorize & remove.

② Remaining  $2^{n-1}$  terms will have  $(\frac{2^{n-1}}{2})$  terms with  $x_2$  &  $(\frac{2^{n-1}}{2})$  minterms will have  $x_2'$  which can also be factorize & remove. —

Continues this process until the last term is left and  $x_n + x_n' = 1$

$$F = (x_n + x_n') \cdot 1 = 1$$

(2.13)

$$F = w'x'y + w'x'y'z + w'y'z + w'y'z' + x'y \quad \text{SOP}$$

a) Truth table:


w	x	y	z	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$= \sum (1, 3, 5, 6, 7, 9, 13, 14, 15)$$

$$\Rightarrow m_1, m_3, m_5, m_6, m_7, m_9, m_{13}, m_{14}, m_{15}$$



b) Logic diagram:

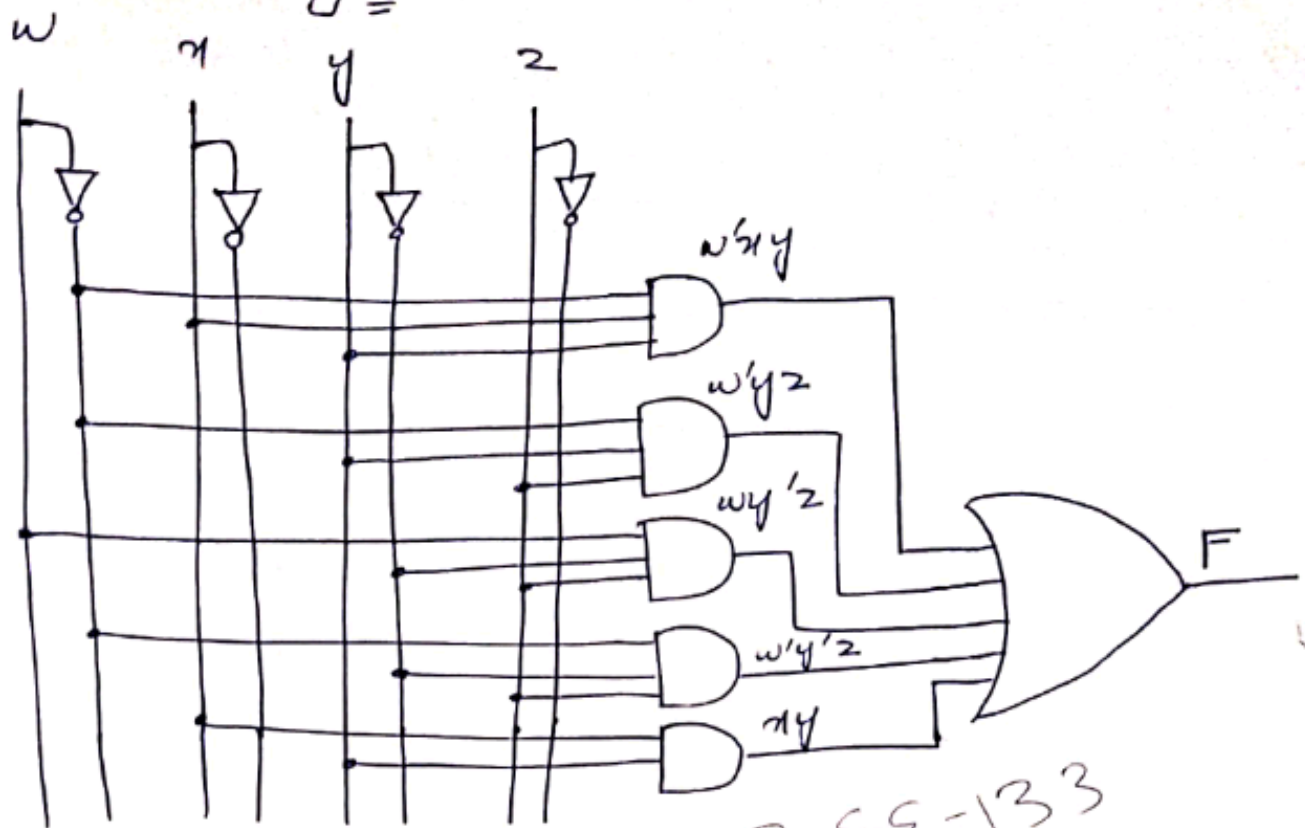

c) Simplify:


$$\begin{aligned}
 &= w'xyz + w'yz + wy'z + w'y'z + xyz \\
 &= (1+w)xyz + w'yz + wy'z + w'y'z \\
 &= xyz + w'yz + wy'z + w'y'z \\
 &= xyz + z(w'y + wy' + w'y') \\
 &= xyz + z(w'(y+y') + wy') \\
 &= xyz + z(w' + wy') \\
 &\Rightarrow xyz + w'z + wy'z
 \end{aligned}$$

BSE-133



e)

$$xy + w'z + wy'z$$

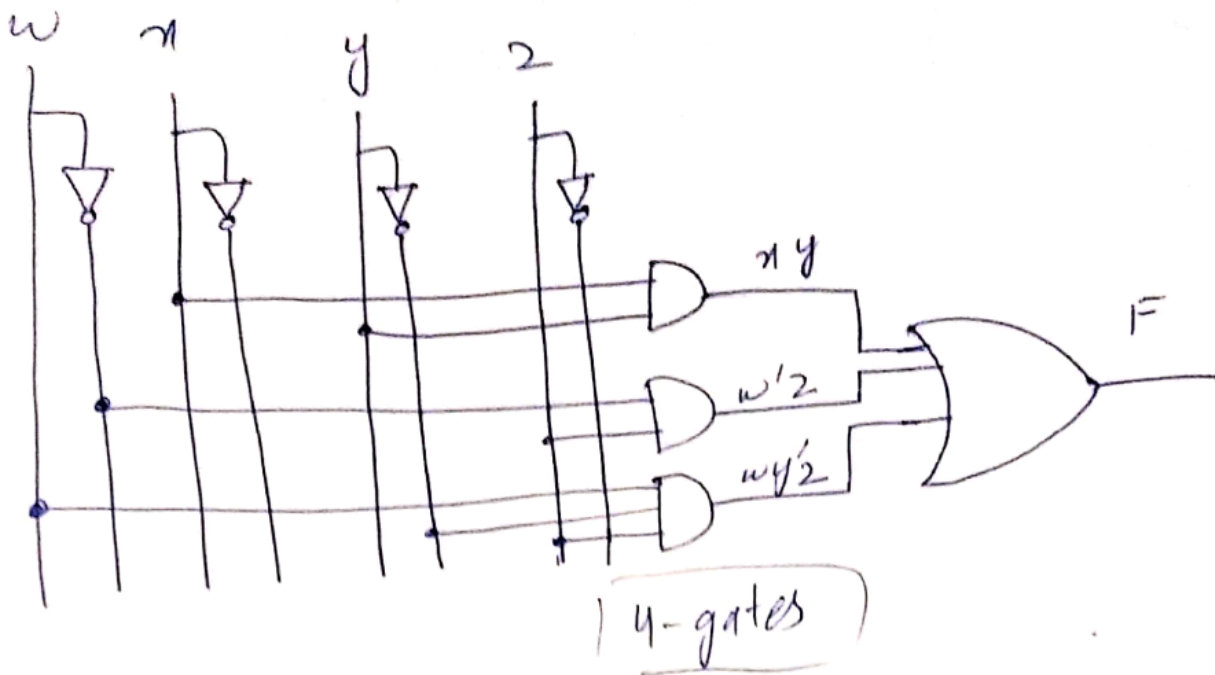

(2.20)

Express the complement in Sum of minterms ( $\Sigma$ ).

a)  $F(w, x, y, z) = \Sigma(1, 5, 7, 11, 12, 14, 15)$

$$F'(w, x, y, z) = \Sigma(0, 2, 3, 4, 6, 8, 9, 10, 13)$$

b)  $F(x, y, z) = \Pi(2, 4, 5)$

$$F'(x, y, z) = \Pi(0, 1, 3, 6, 7) \\ = \Sigma(2, 4, 5)$$

(2.22)

Convert to SOP & POS:

BSC-133

a)  $(w + xy')(x + y'z)$

$$= wx + wy'z + xy' + xy'z$$

$$= wx + wy'z + x(y' + y'z)$$

$$= wx + wy'z + x(y'(1 + z))$$

$$= wx + wy'z + xy'z$$

$$= wx + y'(wz + xz)$$

SOP =  $wx + wy'z + xy'z$

$$= wx(y + y')(z + z') + wy'z(x + x') + xy'z(w + w')$$

$$= (wx + y)(wx + y')(wx + z)(wx + z') + (wy'z + x)$$

$$(wy'z + x')(xy'z + w)(wx + y'z + w')$$

$$= (w + y)(x + y)(w + y')(x + y')(w + z)(x + z)(w + z')$$

$$(x + z')(w + z)(y' + x)(x + z)(x' + w)(x' + y')(x' + z)$$

$$(x + w)(y' + w)(w + z)(w' + x)(w' + y')(w' + z)$$

$$Pos = (w+x)(w+y')(x+y')(x+z)$$

$$b) xy + (w' + y'z')(z' + x'y')$$

$$= xy + w'z' + w'x'y' + y'z' + x'y'z'$$

$$= xy + w'z' + x'(w'y' + y'z') + y'z'$$

$$= xy + w'z' + x'w'y' + y'z' + y'x'$$

$$= xy + w'z' + y'(w'x' + z' + x'z')$$

$$= xy + w'z' + y'(w'x' + z'(1 + x'))$$

$$= xy + w'z' + y'(w'x' + z'x')$$

$$Sop = xy + w'z' + w'x'y' + x'y'z'$$

$$= \cancel{xy(z+z')(w+w') + (w'+y')(w'+z')(x'+z')}(y'+z')$$

$$= \cancel{(x+z)(y+z')(w+w') + (w'+y')(w'+z')}(x'+z')(y'+z')$$

OR

$$= (x + w' + y'z')(y + w' + y'z')(z' + x'y')$$

$$= \cancel{w'}(w' + x + y')(w' + x + z')(w' + y + y')(w' + y + z')(x' + z')(y' + z')$$

$$Pos = \begin{matrix} (w' + x + y')(w' + x + z')w'(w' + y + z')(y' + z')(y' + z') \\ \Rightarrow w'(w' + x + y')(w' + x + z')(w' + y + z')(x' + z')(y' + z') \end{matrix}$$

(2.24)

Find dual:

$$F = x'y + (x+z)(x+y')$$

Using De-morgan's rule

$$= [x'y + (x+z)(x+y')]'$$

$$= (x'y)' [(x+z)(x+y')]'$$

$$= (x+y')(x+z)'(x+y')'$$

$$= (x+y')(x'z' + x'y)$$

Again Applying same rule

$$\text{Dual} \Rightarrow [(x+y')(x'z' + x'y)]'$$

$$= (x+y')' + (x'z' + x'y)'$$

$$= x'y + (x'z')'(x'y)'$$

$$= x'y + (x+z)(x+y')$$

$$F' = \text{Dual of } F$$

(2.26)

Show that +ive logic NAND gate is a -ive logic NOR gate.

Let two +ive NAND) input A & B

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

(-ive NOR)

A	B	Output
1	1	0
1	0	0
0	1	0
0	0	1


Hence, proved by outputs.

BSE-133

(2.28)

write boolean expression & truth table.

(a)

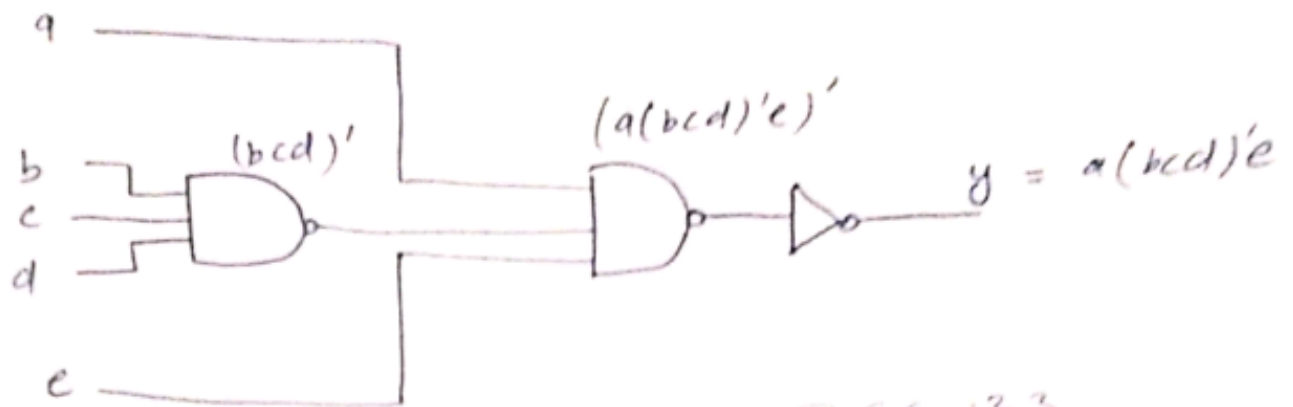

BSE-133

for  $a=0$


b	c	d	e	$(bcd)'$	$y = a(bcd)'e$
0	0	0	0	1	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	1	0



or  $a=1$

b	c	d	e	a	(bcd)'	$a(bcd)'e$
0	0	0	0	1	1	0
0	0	0	1	1	1	1
0	0	1	0	1	1	0
0	0	1	1	1	1	1
0	1	0	0	1	1	0
0	1	0	1	1	1	1
0	1	1	0	1	1	0
0	1	1	1	1	1	1
1	0	0	0	1	1	0
1	0	0	1	1	1	1
1	0	1	0	1	1	0
1	0	1	1	1	1	1
1	1	0	0	1	1	0
1	1	0	1	1	1	1
1	1	1	0	1	1	0
1	1	1	1	1	1	1

(b)

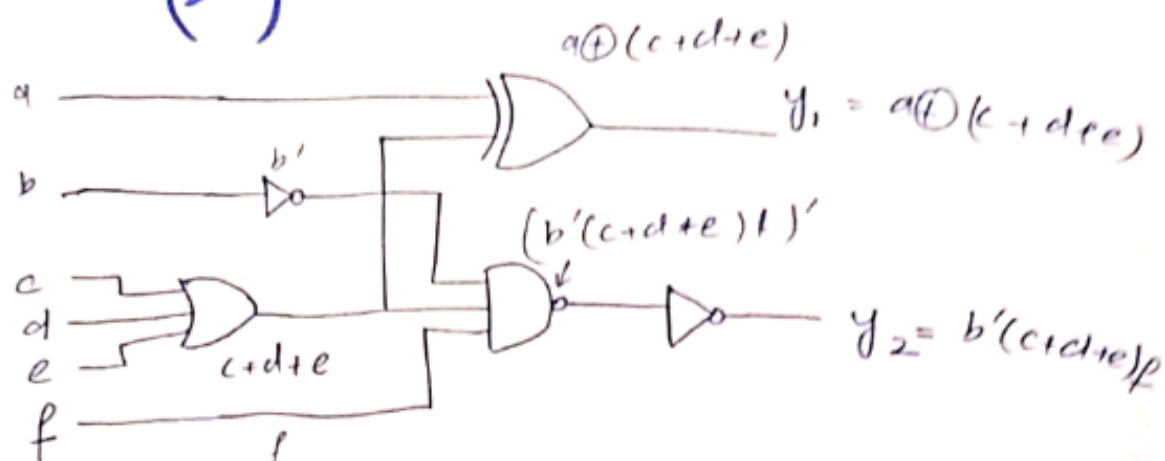

Expression:  $y_1 = a \oplus (c + d + e)$   
 $y_2 = b'(c + d + e)f$

for  $y_1 = a \oplus (c+de) \Rightarrow a \oplus (c+de)$

$2^4 = 8$  rows

a	c	d	e	or c+d+e	y <sub>1</sub> a⊕(c+d+e)
0	0	0	0	0	0
0	0	0	1	1	1
0	0	1	0	1	1
0	0	1	1	1	1
0	1	0	0	1	1
0	1	0	1	1	1
0	1	1	0	1	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	1	0

BSE-133

$$y_2 = b'(c+d+e) \neq$$

$$y_2 = b'(c+d+e) \neq$$

b	c	d	e	f	b'	$\overline{c+d+e}$ <del>b'f</del> c	
0	0	0	0	0	1	0	0
0	0	0	0	1	1	0	0
0	0	0	1	0	1	1	0
0	0	0	1	1	1	1	1
0	0	1	0	0	1	1	0
0	0	1	0	1	1	1	0
0	0	1	1	0	1	1	0
0	0	1	1	1	1	1	0
0	1	0	0	0	1	1	0
0	1	0	0	1	1	1	0
0	1	0	1	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	0	1	0	0
0	1	1	0	1	1	0	0
0	1	1	1	0	1	0	0
0	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0
1	0	0	1	0	0	1	0
1	0	0	1	1	0	1	0
1	0	1	0	0	0	1	0
1	0	1	0	1	0	1	0
1	0	1	1	0	0	1	0
1	0	1	1	1	0	1	0
1	1	0	0	0	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	0	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	0	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	0	0	0	0
1	1	1	1	1	0	0	0

2.30

write in Sum of product form:

$$(w+x+y)(x'+y'+z')$$

$$= wx' + wy' + wz' + xx' + xy' + xz' + x'y + yy' + yz'$$

$$= wx' + wy' + wz' + \bar{x}\bar{y}' + \bar{x}\bar{z}' + x'y + yz'$$


$$= wx'(y+y')(z+z') + wy'(x+x')(z+z') + wz'(x+x')(y+y') + x'y(w+w')(z+z') + yz'(x+x')(w+w')$$

$$= \overset{(1)}{wx'y'z'} + \overset{(2)}{wx'yz} + \overset{(3)}{wx'y'z} + \overset{(4)}{wx'y'z'} + \overset{(5)}{wx'yz'} + \overset{(6)}{wx'y'z'} + \overset{(7)}{wxy'z} + \overset{(8)}{w'xy'z'} + \overset{(9)}{wxy'z'} + \overset{(10)}{w'xy'z'} + \overset{(11)}{wxy'z} + \overset{(12)}{w'xy'z'} + \overset{(13)}{wxy'z'} + \overset{(14)}{w'xy'z'}$$

$$\Rightarrow wx'y'z' + wx'yz + wxy'z + wxy'z' + w'xy'z' + w'xy'z'$$

(2.32) BSGE-133

Show signals

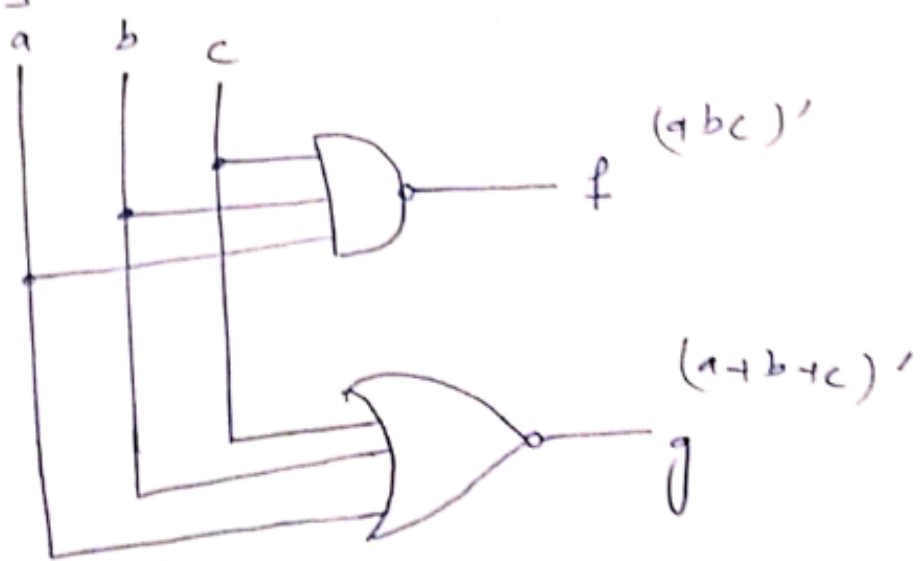

Truth table:

$2^3 = 8 \text{ rows}$

$(abc)'$

$(a+b+c)'$

a	b	c	abc	a+b+c	f	g
0	0	0	0	0	1	1
0	0	1	0	1	1	0
0	1	0	0	1	1	0
0	1	1	0	1	1	0
1	0	0	0	1	1	0
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	0	0

The  
END

BSE-133